

## Assume the Position

Al is repairing the power supply for his stereo, and finds he needs a  $100\ \mu\text{F}$  capacitor rated at 90 V. In his Box o' Caps, he has five  $100\ \mu\text{F}$  capacitors rated at a maximum of 50 V. Can Al fix his stereo with what he has on hand?

